

```
library ieee;
use ieee.std_logic_1164.all;




entity equal is
generic(n : in integer := 8);
port(
a, b : in std_logic_vector(n-1 downto 0);
same : out std_logic);
end equal;

architecture rtl1 of equal is
begin
p0 : process(a,b)
variable same_so_far : std_logic;
begin
same_so_far := '1';
for i in a'range loop --with range attribute, code is
flexi to change width
if(a(i) /= b(i))then
same_so_far := '0';
exit;
end if;
end loop;
same <= same_so_far;
end process;
end rtl1;
```

```
architecture rtl2 of equal is
signal eachbit : std_logic_vector(a'length-1 downto 0);
begin
xnor_gen : for i in a'range generate
eachbit(i) <= not (a(i) xor b(i));
end generate;

p0:process(eachbit)
variable bitsame : std_logic;
begin
bitsame := eachbit(0);
for i in 1 to a'length-1 loop
bitsame := bitsame and eachbit(i);
end loop;
same <= bitsame;
end process;
end rtl2;
```
 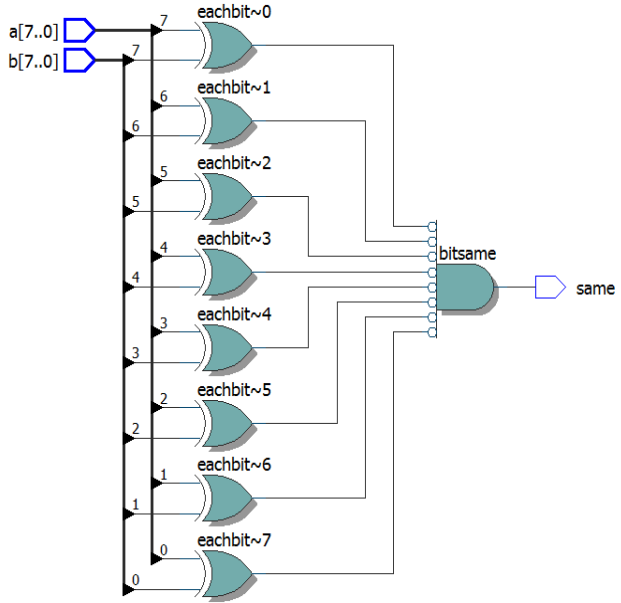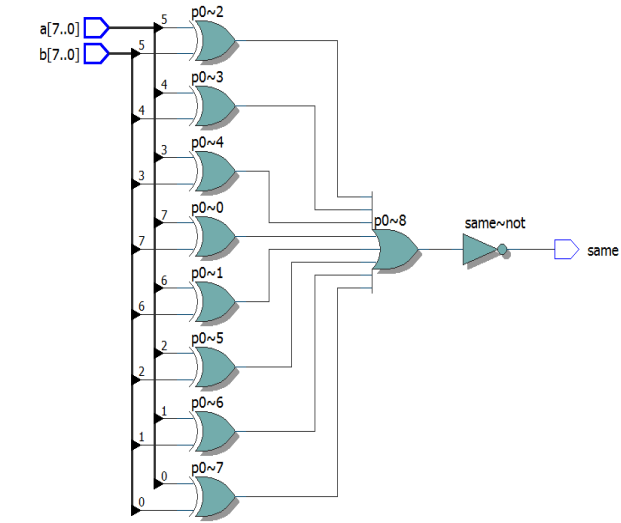
```
architecture rtl3 of equal is
begin
same <= '1' when a = b else '0';
end rtl3;
```



```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;
```

```
entity tbequal is
end entity;
```

```
architecture beh of tbequal is
```

```
component equal
generic(n : in integer := 8);
port(
a, b : in std_logic_vector(n-1 downto 0);
same : out std_logic);
end component;
```

```
constant w : integer := 5; --signal width
signal a, b : std_logic_vector(w-1 downto 0);
signal y, y1, y2, y3 : std_logic;
```

```
constant period : time := 50ns;
constant strobe : time := period - 5ns;
```

```
begin
p0 : process
begin
for j in 0 to 2**w-1 loop
a <= conv_std_logic_vector(j,w);
for k in 0 to 2**w-1 loop
b <= conv_std_logic_vector(k,w);
wait for period;
end loop;
end loop;
wait;
end process;

y <= '1' when a = b else '0';
check : process
variable err_cnt : integer := 0;
begin
wait for strobe;
for j in 1 to 2**(w*2) loop
if(y /= y1) or (y /= y2) or (y /= y3) then
assert false report "not compare" severity warning;
err_cnt := err_cnt +1;
end if;
wait for period;
end loop;
assert (err_cnt = 0) report "test failed" severity error;
assert (err_cnt = 0) report "test passed" severity note;
wait;
end process;
```

```
equal1 : equal
generic map(n => w)
port map(a => a, b => b, same => y1);
equal2 : equal
generic map(n => w)
port map(a => a, b => b, same => y2);
equal3 : equal
generic map(n => w)
port map(a => a, b => b, same => y3);
```

```
end beh;
```

```
configuration cfg_tbequal of tbequal is
for beh
for equal1 : equal
use entity work.equal(rtl1);
end for;
for equal2 : equal
use entity work.equal(rtl2);
end for;
for equal3 : equal
use entity work.equal(rtl3);
```

```
    end for;  
end for;  
end cfg_tbeqal;
```